

Wetterstation: Bauvorschlag 2 Sender

R1 = 10k Ω

Pinbelegung:

Arduino	DHT11
GND	GND am DHT11
VCC	R1 VCC am DHT11
13	R1 Data am DHT11
Arduino	Sender
3	DATA
VCC	VCC
GND	GND

