

Wetterstation: Binaer mit Breadboard

$$R1 - R8 = 220 \, \Omega$$

Pinbelegung:

Arduino	LEDs
5	R1 → LED1
6	R2 → LED2
7	R3 → LED3
8	R4 → LED4
9	R5 → LED5
10	R6 → LED6
11	R7 → LED7
12	R8 → LED8
GND	GND von LED1 – LED8

