

Wetterstation: DHT11 4x7 mit Breadboard

R1 – R4 = 1 k Ω

R5 = 10 k Ω

Pinbelegung:

Arduino	Breadboard & Display
2	R1 → Kontakt 1
3	R2 → Kontakt 2
4	R3 → Kontakt 3
5	R4 → Kontakt 4
6	Kontakt a
7	Kontakt b
8	Kontakt c
9	Kontakt d
10	Kontakt e
11	Kontakt f
12	Kontakt g
13	Kontakt h
A0	DATA am DHT11 & R5
VCC	VCC am DHT11 & R5
GND	GND am DHT11

